

21. HALF ADDER

EXP.NO: 21

AIM: To design and implement the two bit half adder using Logisim simulator.

PROCEDURE:


- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the XOR gate and AND gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.

TRUTH TABLE:

a	b	x	y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Logical Diagram:
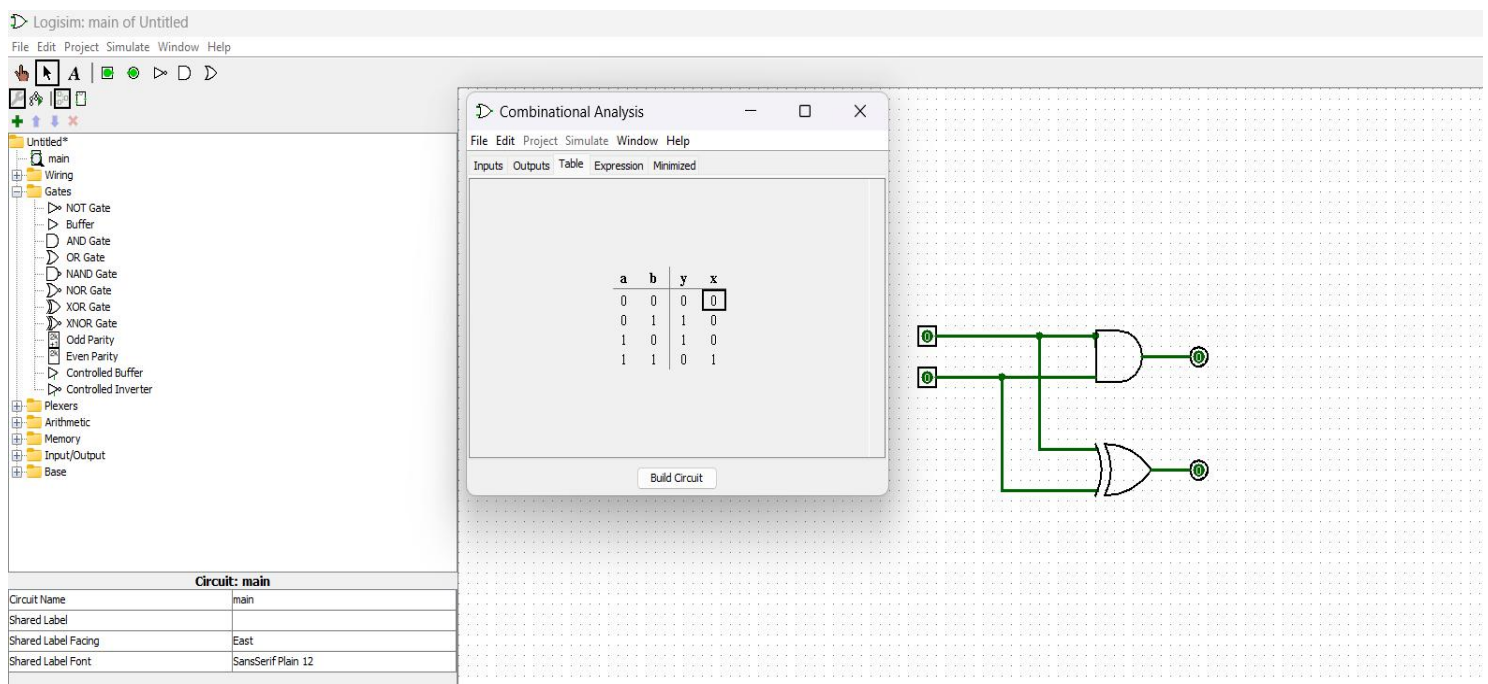
$$S = A \text{ XOR } B \quad C = A \text{ AND } B$$



RESULT: Thus 2-bit half adder has been implemented successfully using logisim simulator.