#### 22. TWO BIT HALF SUBTRACTOR

### **EXP.NO: 22**

AIM: To design and implement the two bit half subtractor using Logisim simulator.

### **PROCEDURE:**

- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the OR gate, AND gate and NOT gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.


## **TRUTH TABLE:**

a	b	Х	У
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Diff=A'B+AB'

Borrow = A'B

# **Logical Diagram:**

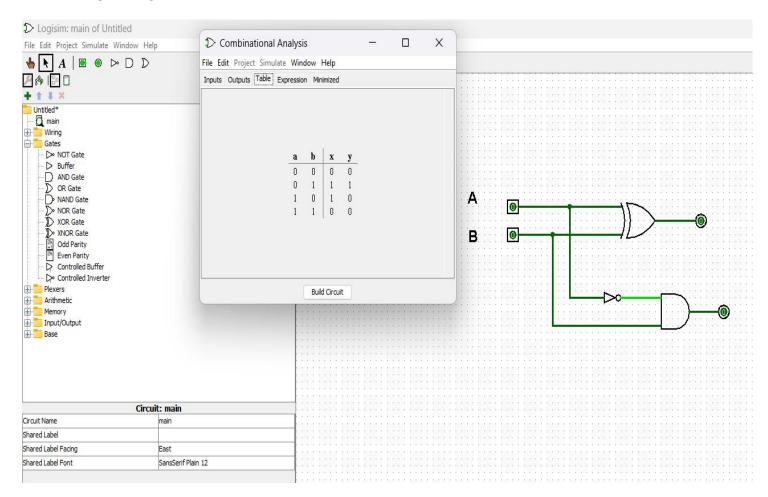

RESULT: Thus 2-bit half subtractor has been designed and implemented successfully using logisim simulator.